

## Solution

**EXAMPLE 1.5 :** The resistance of a certain length of wire is  $4.6 \, \Omega$  at  $20^\circ\text{C}$  and  $5.68 \, \Omega$  at  $80^\circ\text{C}$ . Determine (a) temperature co-efficient of resistance of the material of wire at  $0^\circ\text{C}$  (b) resistance of wire at  $60^\circ\text{C}$ .

**SOLUTION :**

$$\begin{aligned} R_1 &= 5.68 \, \Omega & t_1 &= 80^\circ\text{C} \\ R_2 &= 4.6 \, \Omega & t_2 &= 20^\circ\text{C} \end{aligned}$$

(a)  $\frac{R_2}{R_1} = \frac{1 + \alpha_0 t_2}{1 + \alpha_0 t_1}$

$$\frac{4.6}{5.68} = \frac{1 + \alpha_0 (20)}{1 + \alpha_0 (80)}$$

$$0.8098 + 64.79 \alpha_0 = 1 + 20 \alpha_0$$

$$44.79 \alpha_0 = 0.1902$$

$$\alpha_0 = 0.00425 / ^\circ\text{C}$$

(b)  $\frac{R_2}{R_3} = \frac{1 + \alpha_0 t_2}{1 + \alpha_0 t_1}$

$$\frac{4.6}{R_3} = \frac{1 + \alpha_0 t_2}{1 + \alpha_0 t_1}$$

$$\frac{4.6}{R_3} = \frac{1 + (0.00425)(20)}{1 + (0.00425)(60)}$$

$$R_3 = 4.6 \times \frac{1.255}{1.085}$$

$$R_3 = 5.3 \, \Omega$$

**EXAMPLE 1.6 :** The resistance of a wire of  $3 \, \text{mm}^2$  cross sectional area and 6 m length is  $0.15 \, \Omega$  at  $0^\circ\text{C}$ . When the temperature of the wire is raised to  $65^\circ\text{C}$  the resistance is found to be  $0.2 \, \Omega$ . Calculate the temperature co-efficient of resistance of the wire and its resistivity at  $0^\circ\text{C}$ .

**SOLUTION :**

$$a = 3 \, \text{mm}^2 = 3 \times 10^{-6} \, \text{m}^2$$

$$l = 6 \, \text{m}$$

$$R_0 = 0.15 \, \Omega$$

$$\therefore R_0 = \rho_0 \frac{l}{a}$$

$$0.15 = \rho_0 \times \frac{6}{3 \times 10^{-6}}$$

$$\rho_0 = 7.5 \times 10^{-8} \, \Omega\text{m}$$

$$\frac{R_2}{R_1} = \frac{1 + \alpha_0 t_2}{1 + \alpha_0 t_1}$$

$$\frac{0.15}{0.2} = \frac{1 + (\alpha_0)(0)}{1 + (\alpha_0)(65)}$$

$$0.15 (1 + 65 \alpha_0) = 0.2$$

$$\alpha_0 = 0.005 / ^\circ\text{C}$$

**EXAMPLE 1.8 :** A copper wire has a resistivity of  $1.6 \times 10^{-6} \Omega\text{-cm}$  at  $0^\circ\text{C}$  and at  $20^\circ\text{C}$ , the temperature co-efficient of resistance is  $1/254.5^\circ\text{C}^{-1}$ . Find the resistivity and temperature co-efficient of resistance at  $60^\circ\text{C}$ .

**SOLUTION :**

$$\rho_0 = 1.6 \times 10^{-6} \Omega\text{ cm}$$

$$\alpha_{20} = 1/254.5^\circ\text{C}^{-1}$$

$$\alpha_{20} = \frac{\alpha_0}{1 + \alpha_0 t}$$

$$1/254.5 = \frac{\alpha_0}{1 + 20\alpha_0}$$

$$3.929 \times 10^{-3} (1 + 20 \alpha_0) = \alpha_0$$

$$0.92 \alpha_0 = 3.929 \times 10^{-3}$$

$$\alpha_0 = 4.27 \times 10^{-3}$$

$$\alpha_0 = 1/234.19^\circ\text{C}^{-1}$$

$$\rho_{60} = \rho_0 [1 + \alpha_0 t]$$

$$= 1.6 \times 10^{-6} [1 + 4.27 \times 10^{-3} \times 60]$$

$$= 1.6 \times 10^{-6} (1.2562)$$

$$= 2.01 \times 10^{-6} \Omega\text{-cm}$$


$$\alpha_{60} = \frac{\alpha_0}{1 + \alpha_0 t}$$

$$= \frac{4.27 \times 10^{-3}}{1 + 4.27 \times 10^{-3} \times 60}$$

$$= 3.399 \times 10^{-3}^\circ\text{C}^{-1}$$

$$= \frac{1}{294.2}^\circ\text{C}^{-1}$$


**EXAMPLE 1.25 :** Find the current supplied by the battery in the network shown in the Fig. E.1.25(a).

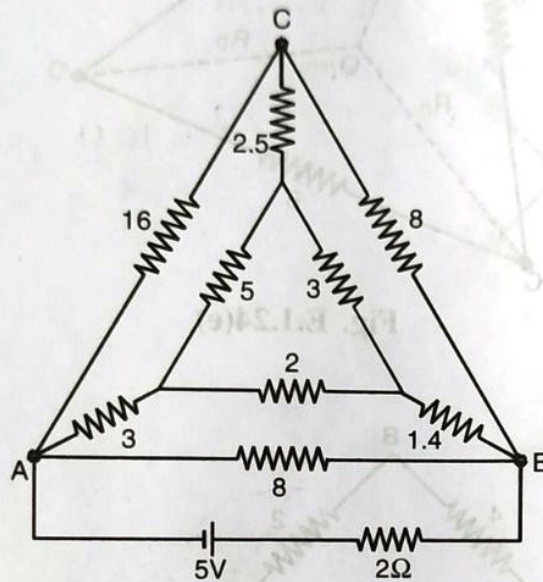

**Fig. E.1.25(a)**

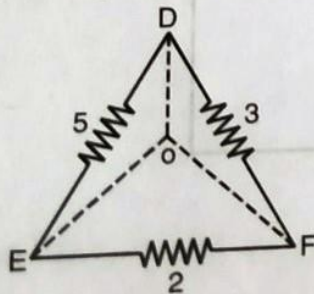**SOLUTION :**

Converting the inner delta to its equivalent star




$$OD = \frac{5 \times 3}{10} = 1.5 \, \Omega$$

$$OE = \frac{5 \times 2}{10} = 1 \, \Omega$$

$$OF = \frac{3 \times 2}{10} = 0.6 \, \Omega$$



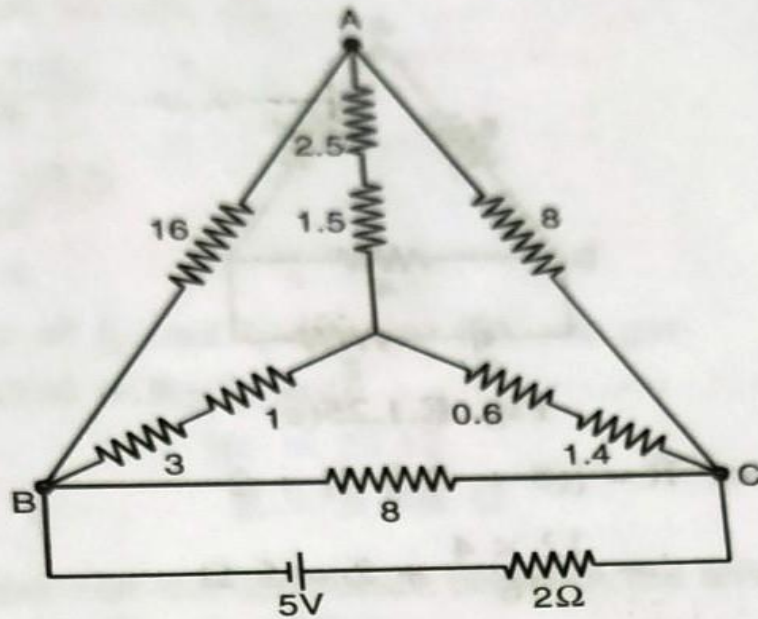

**Fig. E.1.25(c)**


Now converting star ABC to delta

$$AB = \frac{4 \times 4 + 4 \times 2 + 4 \times 2}{2} = 16 \, \Omega$$

$$BC = \frac{32}{4} = 8 \, \Omega$$

$$CA = \frac{32}{4} = 8 \, \Omega$$

Thus, the circuit reduces to

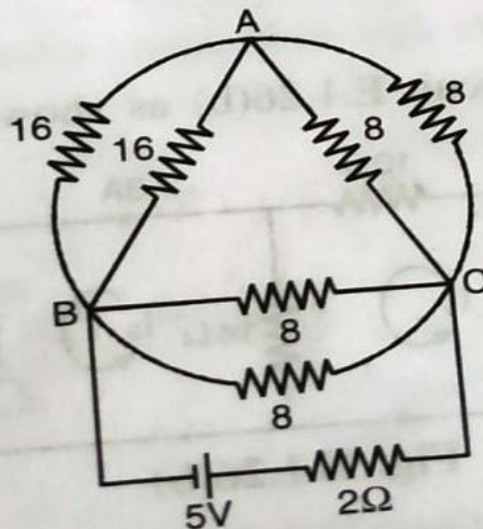

This is further simplified as below :

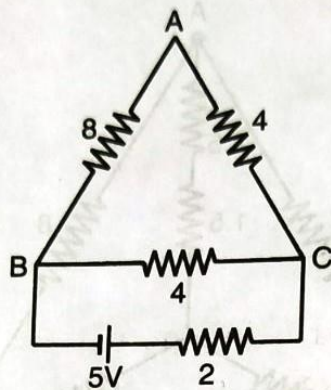



Fig. E.1.25(e)

$$\begin{aligned} \text{Now total resistance } R &= [(8 + 4) \parallel 4] + 2 \\ &= \frac{12 \times 4}{16} + 2 = 5 \Omega \end{aligned}$$

$$\therefore I = \frac{5}{5} = 1 \text{ A}$$


**EXAMPLE 1.29 :** Determine equivalent resistance between terminals A and B of network shown in fig. E.1.29(a).

(GTU June 2009)

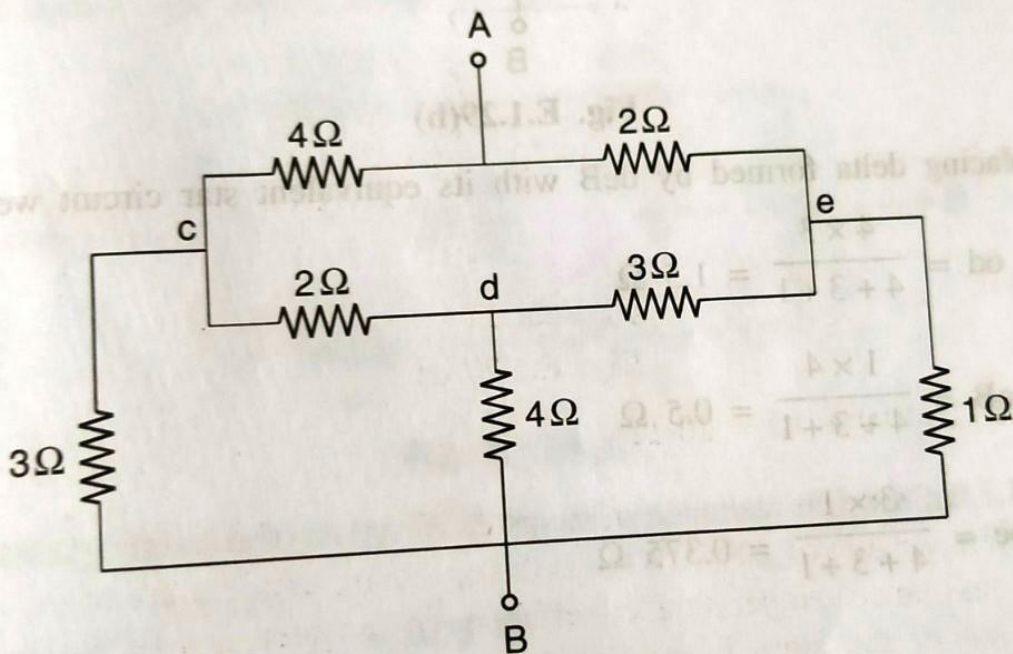

**SOLUTION :**

Redrawing the given circuit as shown below we get

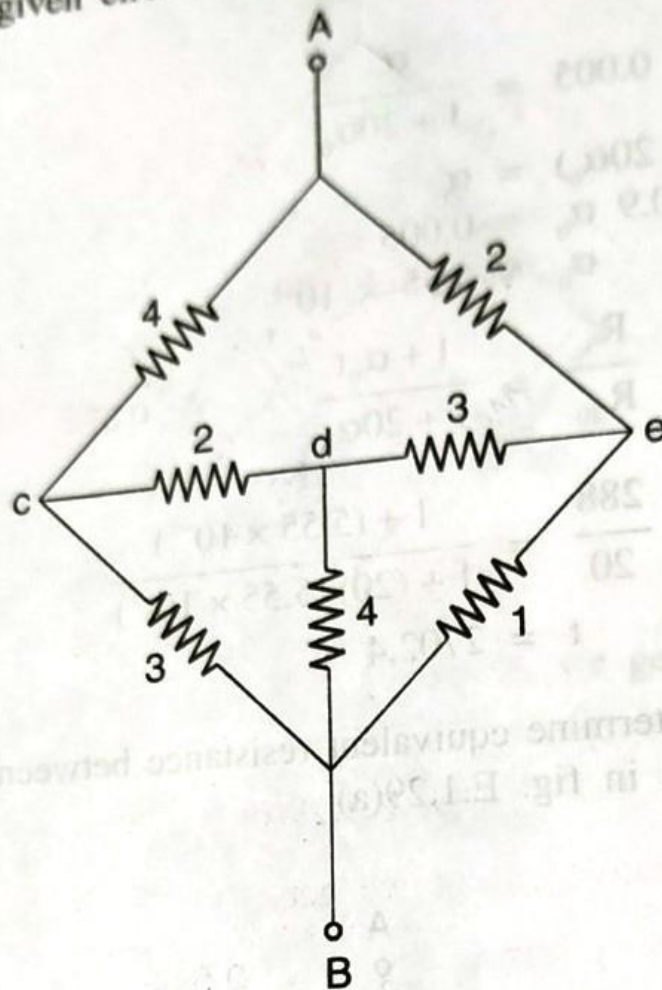

**Fig. E.1.29(b)**

Replacing delta formed by deB with its equivalent star circuit

$$o_d = \frac{4 \times 3}{4 + 3 + 1} = 1.5 \, \Omega$$

$$o_B = \frac{1 \times 4}{4 + 3 + 1} = 0.5 \, \Omega$$

$$o_e = \frac{3 \times 1}{4 + 3 + 1} = 0.375 \, \Omega$$



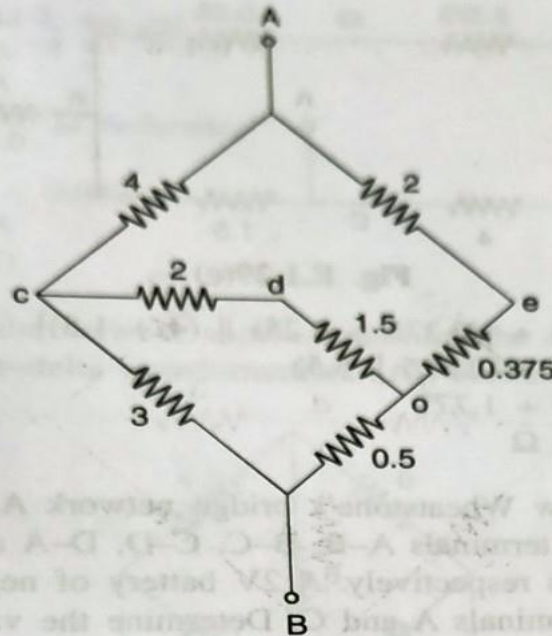


Fig. E.1.29(c)

If we redraw the above circuit we get

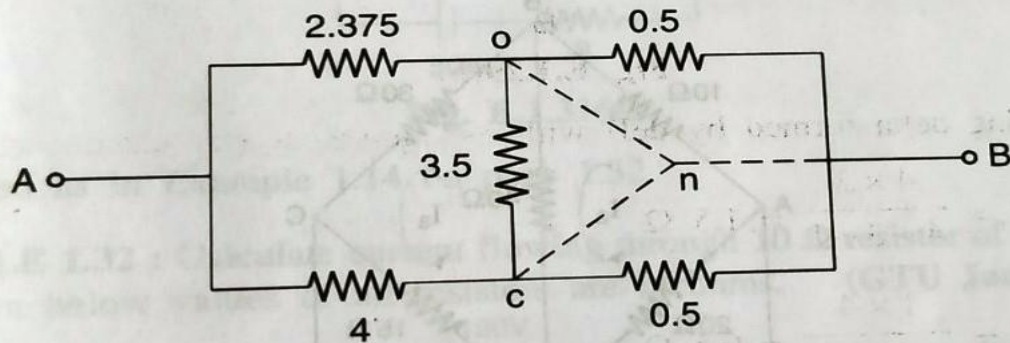



Fig. E.1.29(d)

Replacing delta formed by OCB by its equivalent star we get

$$o_n = \frac{3.5 \times 0.5}{3.5 + 0.5 + 3} = 0.25 \, \Omega$$

$$B_n = \frac{0.5 \times 3}{3.5 + 0.5 + 3} = 0.214 \, \Omega$$

$$C_n = \frac{3 \times 3.5}{3.5 + 0.5 + 3} = 1.5 \, \Omega$$

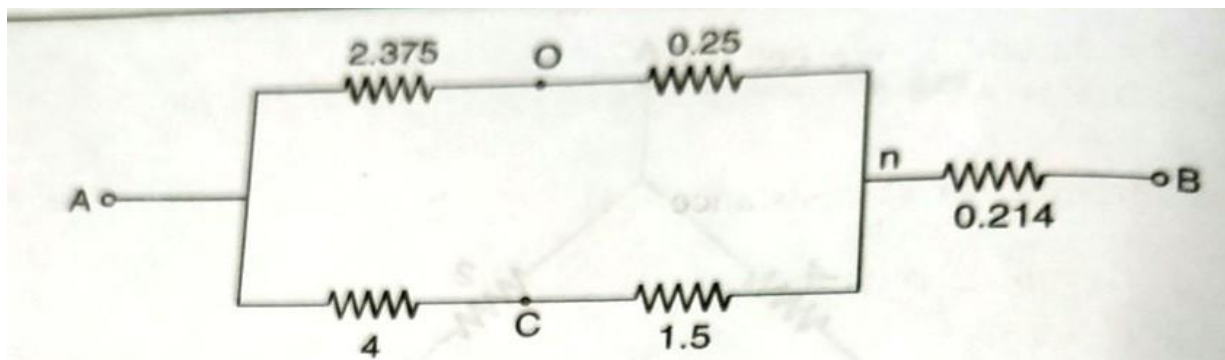


**Fig. E.1.29(e)**

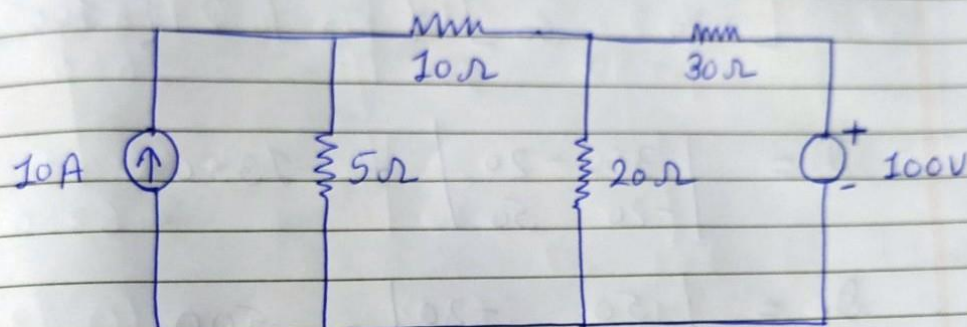
$$\begin{aligned}
 R_{AB} &= 0.214 + [(2.375 + 0.25) \parallel (4 + 1.5)] \\
 &= 0.214 + (2.625 \parallel 5.5) \\
 &= 0.214 + 1.777 \\
 &= 1.991 \, \Omega
 \end{aligned}$$



7) For the circuit below determine the voltage across the  $20\Omega$  resistor using mesh analysis.



Sol<sup>n</sup>  
=

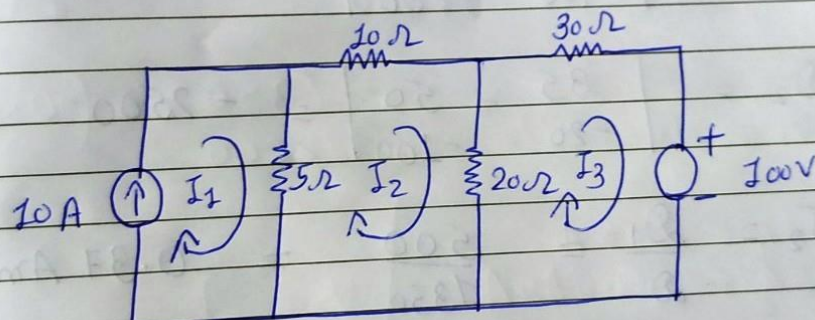

$$\therefore I_1 = 10 \text{ A}$$

Applying KVL in mesh-2

$$0 = -5I_1 + 35I_2 - 20I_3$$

$$\text{Put } I_1 = 10 \text{ A}$$

$$\therefore 35I_2 - 20I_3 = 50 \quad \text{--- (1)}$$

Applying KVL in mesh-3

$$\therefore 50I_3 - 20I_2 = -100 \quad \dots (2)$$

Apply Cramer's rule

$$\begin{bmatrix} 35 & -20 \\ -20 & 50 \end{bmatrix} \begin{bmatrix} I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 50 \\ -100 \end{bmatrix}$$

$$\therefore D = \begin{vmatrix} 35 & -20 \\ -20 & 50 \end{vmatrix} = 1350$$

$$\therefore D_1 = \begin{vmatrix} 50 & -20 \\ -100 & 50 \end{vmatrix} = 500$$

$$\therefore D_2 = \begin{vmatrix} 35 & 50 \\ -20 & -100 \end{vmatrix} = -2500$$

$$\therefore I_2 = \frac{D_1}{D} = \frac{500}{1350} = 0.37 \text{ Amp}$$

$$\therefore I_3 = \frac{D_2}{D} = \frac{-2500}{1350} = -1.85 \text{ Amp}$$

Voltage across  $200 \Omega$  is


$$V_{200} = (I_2 - I_3) 20$$

$$= (0.37 + 1.85) \times 20$$

$$V_{200} = 44.4 \text{ V}$$



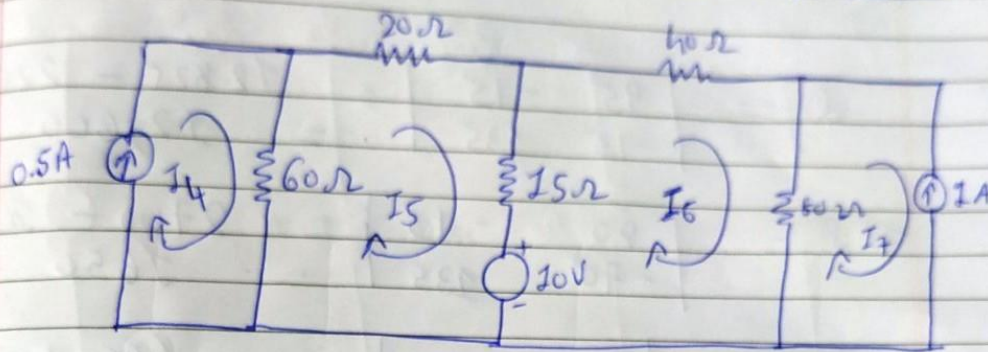Q. Using mesh analysis find currents  $I_1$ ,  $I_2$  and  $I_3$  for given circuit in fig. below.



Sol<sup>n</sup>

$$\therefore I_1 = 0.5 \text{ A} \quad \& \quad I_3 = -1 \text{ A}$$

Apply KVL in mesh-2

$$\therefore 20 I_2 + 15 (I_2 - I_3) + 60 (I_2 - I_1) = (-10)$$

$$\therefore 20 I_2 + 15 (I_2 - I_3) + 60 (I_2 - 0.5) = -10$$

$$\therefore 95 I_2 - 15 I_3 = -10 + 30$$

$$\therefore 95 I_2 - 15 I_3 = 20 \quad \text{--- (1)}$$

Apply KVL in mesh-3

$$\therefore 40 I_3 + 80 (I_3 - I_2) + 15 (I_3 - I_2) = 10$$

$$\therefore 135 I_3 - 80 I_2 - 15 I_2 = 10$$

$$\therefore 135 I_3 - 95 I_2 = -70 \quad \text{--- (2)}$$



$$\begin{bmatrix} 95 & -15 \\ -15 & 135 \end{bmatrix} \begin{bmatrix} I_5 \\ I_6 \end{bmatrix} = \begin{bmatrix} 20 \\ -70 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 95 & -15 \\ -15 & 135 \end{vmatrix} = 12825 - 225 = 12600$$

$$\Delta_1 = \begin{vmatrix} 20 & -15 \\ -70 & 135 \end{vmatrix} = 2700 - 1050 = 1650$$

$$\Delta_2 = \begin{vmatrix} 95 & 20 \\ -15 & -70 \end{vmatrix} = -6650 + 300 = -6350$$

$$I_5 = \frac{\Delta_1}{\Delta} = \frac{1650}{12600} = (0.130) \text{ A}$$

$$I_6 = \frac{\Delta_2}{\Delta} = \frac{-6350}{12600} = (-0.50) \text{ A}$$


$$I_4 = 0.5 \text{ A}$$

$$I_5 = 0.130 \text{ A}$$

$$I_6 = -0.50 \text{ A}$$

$$I_7 = -1 \text{ A}$$

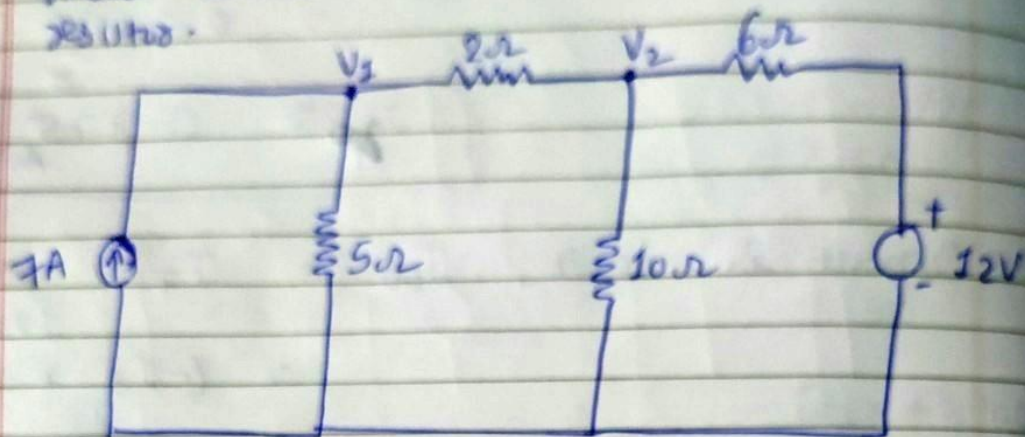- ⑨ For the circuit of fig. below determine the nodal voltages and current through  $2\Omega$  resistor.



Sol<sup>n</sup> Apply KCL at node - 1

$$\frac{V_1}{5} + \frac{V_1 - V_2}{2} = 7 \quad \text{--- (1)}$$

$$\therefore \frac{V_1}{5} + \frac{V_1}{2} - \frac{V_2}{2} = 7$$

$$\therefore 0.2V_1 + 0.5V_1 - 0.5V_2 = 7$$

$$\therefore 0.7V_1 - 0.5V_2 = 7 \quad \text{--- (1)}$$

Apply KCL at node - 2

$$\frac{V_2 - V_1}{2} + \frac{V_2}{10} + \frac{V_2 - 12}{6} = 0$$



$$\therefore \frac{V_2}{2} - \frac{V_1}{2} + \frac{V_2}{10} + \frac{V_2}{6} - 2 = 0$$

$$\therefore 0.5V_2 - 0.5V_1 + 0.1V_2 + 0.16V_2 = 2$$

$$\therefore 0.76V_2 - 0.5V_1 = 2 \quad \text{--- (2)}$$

$$\therefore \begin{bmatrix} 0.7 & -0.5 \\ -0.5 & 0.76 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 7 \\ 2 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.7 & -0.5 \\ -0.5 & 0.76 \end{vmatrix} = 0.532 - 0.25 = \cancel{0.282} \quad 0.282$$

$$\Delta_1 = \begin{vmatrix} 7 & -0.5 \\ 2 & 0.76 \end{vmatrix}$$

$$= \cancel{5.32} + 1 = \cancel{6.032}$$


$$\Delta_2 = \begin{vmatrix} 0.7 & 7 \\ -0.5 & 2 \end{vmatrix} = 1.4 + 3.5 = 4.9$$

$$\therefore V_1 = \frac{\Delta_1}{\Delta} = \frac{\cancel{6.032}}{0.282} = \frac{22.41}{\cancel{6.032}} \text{ Volt}$$

$$\therefore V_2 = \frac{\Delta_2}{\Delta} = \frac{4.9}{0.282} = \underline{\underline{17.375 \text{ Volt}}}$$



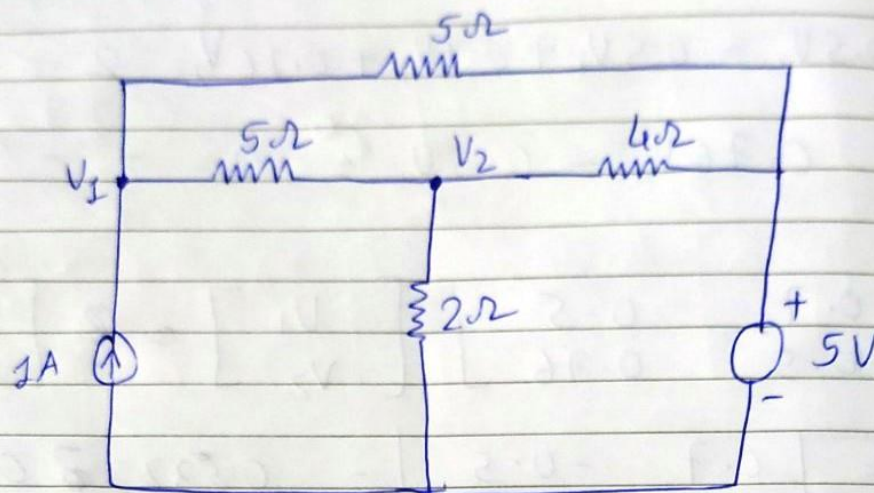- 10) For the circuit of fig below determine the  $V_1$  and  $V_2$  nodal voltages.



Sol<sup>n</sup>:- Apply KCL at node-1

$$\frac{V_1 - V_2}{5} + \frac{V_1 - 5}{5} = 1$$

$$\frac{V_1}{5} - \frac{V_2}{5} + \frac{V_1}{5} - 1 = 1$$

$$\therefore \frac{2}{5} V_1 - \frac{V_2}{5} = 2$$

$$\therefore 0.4 V_1 - 0.2 V_2 = 2 \quad \text{--- (i)}$$

APPLY KCL at node-2

$$\frac{V_2}{2} + \frac{V_2 - V_1}{5} + \frac{V_2 - 1.25}{4} = 0$$

$$\frac{V_2}{2} + \frac{V_2}{5} - \frac{V_1}{5} + \frac{V_2}{4} - 1.25 = 0$$

$$0.5 V_2 + 0.2 V_2 - 0.2 V_1 + 0.25 V_2 = 1.25$$

$$0.95 V_2 - 0.2 V_1 = 1.25 \quad \dots (2)$$

$$\begin{bmatrix} 0.4 & -0.2 \\ -0.2 & 0.95 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ 1.25 \end{bmatrix}$$

$$\Delta = \begin{vmatrix} 0.4 & -0.2 \\ -0.2 & 0.95 \end{vmatrix} = 0.38 - 0.04 = 0.34$$

$$\Delta_1 = \begin{vmatrix} 2 & -0.2 \\ 1.25 & 0.95 \end{vmatrix} = 1.90 + 0.25 = 2.15$$

$$\Delta_2 = \begin{vmatrix} 0.4 & 2 \\ -0.2 & 1.25 \end{vmatrix} = 0.5 + 0.4 = 0.9$$

$$V_1 = \frac{\Delta_1}{\Delta} = \frac{2.15}{0.34} = \underline{\underline{6.32 \text{ V}}}$$

$$V_2 = \frac{\Delta_2}{\Delta} = \frac{0.9}{0.34} = \underline{\underline{2.64 \text{ V}}}$$



**EXAMPLE 2.2 :** Two metal plates of area  $100 \text{ cm}^2$  are separated by a dielectric of  $2 \text{ mm}$  having a relative permittivity of  $5$ . When a dc voltage of  $500\text{V}$  is applied across the capacitor plates, find (i) capacitance (ii) charge on the capacitor (iii) electric field strength and (iv) electric flux density.

**SOLUTION :**

$$A = 100 \text{ cm}^2, \quad d = 2 \text{ mm}, \quad \epsilon_r = 5, \quad V = 500 \text{ V}$$

$$(i) \quad C = \frac{\epsilon_r \epsilon_0 A}{d}$$

$$= \frac{5 \times 8.854 \times 10^{-12} \times 100 \times 10^{-4}}{2 \times 10^{-3}}$$

$$= 221.35 \times 10^{-12} \text{ F}$$

$$= 221.35 \text{ pF}$$

$$(ii) \quad Q = CV$$

$$= 221.35 \times 10^{-12} \times 500$$

$$= 0.1107 \times 10^{-6} \text{ C}$$

$$(iii) \quad E = \frac{V}{d}$$

$$= \frac{500}{2 \times 10^{-3}}$$

$$= 250 \times 10^3 \text{ V/m}$$

$$= 250 \text{ KV/m}$$

$$(iv) \quad D = \frac{Q}{A}$$

$$= \frac{0.1107 \times 10^{-6}}{100 \times 10^{-4}}$$


$$= 11.07 \text{ } \mu\text{C/m}^2$$



**EXAMPLE 2.4 :** A capacitor is made up of two plates with an area of  $11 \text{ cm}^2$  which are separated by a mica sheet  $2 \text{ mm}$  thick. If the relative permittivity of mica is  $6$ , find its capacitance. Now, if one plate is moved further to give an air gap  $0.5 \text{ mm}$  wide between the plate and mica, find the new capacitance.

(G.U. Nov. 2005)

**SOLUTION :**

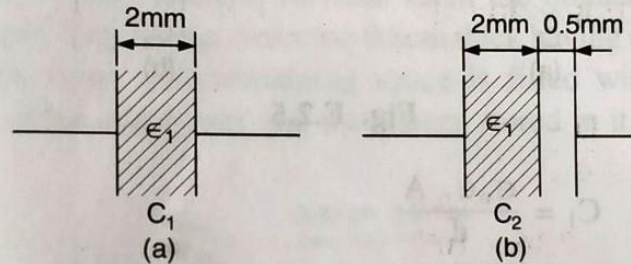

**Fig. E.2.4**

$$A = 11 \text{ cm}^2 = 11 \times 10^{-4} \text{ m}^2, \quad d = 2 \text{ mm} = 2 \times 10^{-3} \text{ m}, \quad \epsilon_r = 6$$


Refer Fig. E.2.4(a).

$$\begin{aligned} C &= \frac{\epsilon_0 \epsilon_r A}{d} \\ &= \frac{8.854 \times 10^{-12} \times 6 \times 11 \times 10^{-4}}{2 \times 10^{-3}} \\ &= 29.21 \times 10^{-12} \text{ F} \\ &= 29.21 \text{ pF} \end{aligned}$$

$$\begin{aligned} C &= \frac{\epsilon_0 A}{\frac{d_1}{\epsilon_1} + \frac{d_2}{\epsilon_2}} \\ &= \frac{8.854 \times 10^{-12} \times 11 \times 10^{-4}}{\frac{2 \times 10^{-3}}{6} + \frac{0.5 \times 10^{-3}}{1}} \\ &= 11.68 \times 10^{-12} \text{ F} \\ &= 11.68 \text{ pF} \end{aligned}$$

**EXAMPLE 2.7 :** Two plates are kept 1.5 cm apart in air and 1 kV supply is connected across them. Calculate the electric field strength in air when a glass sheet 0.5 cm thick with relative permittivity 3 is introduced between the plates without changing the previous distance between the plates.

**SOLUTION :**

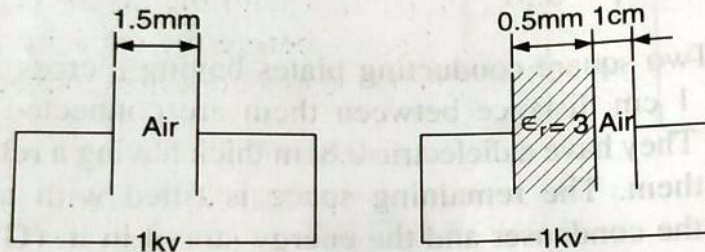

**Fig. E.2.7**

$$d = 1.5 \text{ cm}, \quad V = 1 \text{ kV}, \quad d_g = 0.5 \text{ cm}, \quad \epsilon_{r_g} = 3, \quad d_{\text{air}} = 1 \text{ cm}, \quad \epsilon_{r_{\text{air}}} = 1$$

$$\begin{aligned} C &= \frac{\epsilon_o A}{\frac{d_{\text{air}}}{\epsilon_{r_{\text{air}}}} + \frac{d_g}{\epsilon_{r_g}}} \\ &= \frac{8.854 \times 10^{-12} \times A}{1 \times 10^{-12} + \frac{0.5 \times 10^{-2}}{3}} \\ &= 7.589 \times 10^{-10} \times A \quad \text{farads} \end{aligned}$$

$$Q = CV$$

$$= 7.589 \times 10^{-10} \times A \times 1000 \text{ C}$$

$$= 7.589 \times 10^{-7} \times A \text{ C}$$

$$D = \frac{Q}{A}$$

$$= \frac{7.589 \times 10^{-7} \text{ A}}{A}$$

$$= 7.589 \times 10^{-7} \text{ C/m}^2$$

$$E_{\text{air}} = \frac{D}{\epsilon_0}$$

$$= \frac{7.589 \times 10^{-7}}{8.854 \times 10^{-12}}$$

$$= 85712.67 \text{ V/m}$$

$$= 85.712 \text{ kV/m}$$