

## Assignment 1

**Institute: DEPSTAR**

**Branch: CSE Div:2**

- The resistance of a certain length of wire is  $4.6 \Omega$  at  $20^\circ\text{C}$  and  $5.68 \Omega$  at  $80^\circ\text{C}$ . Determine
  - temperature co-efficient of resistance of the material of wire at  $0^\circ\text{C}$
  - resistance of wire at  $60^\circ\text{C}$ .
- The resistance of a wire of  $3 \text{ mm}^2$  cross sectional area and 6 m length is  $0.15 \Omega$  at  $0^\circ\text{C}$ . When the temperature of the wire is raised to  $65^\circ\text{C}$  the resistance is found to be  $0.2 \Omega$ . Calculate the temperature co-efficient of resistance of the wire and its resistivity at  $0^\circ\text{C}$ .
- A copper wire has a resistivity of  $1.6 \times 10^{-6} \Omega\text{-cm}$  at  $0^\circ\text{C}$  and at  $20^\circ\text{C}$ , the temperature co efficient of resistance is  $1/254.5^\circ\text{C}^{-1}$  Find the resistivity and temperature co-efficient of resistance at  $60^\circ\text{C}$ .
- Find the current supplied by the battery in the network shown below in figure-1 by using star delta transformation.

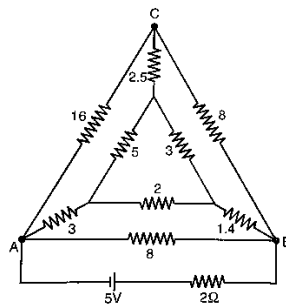


Figure -1

- Determine equivalent resistance between terminal A and B shown in network (figure-2) by using star delta transformation.

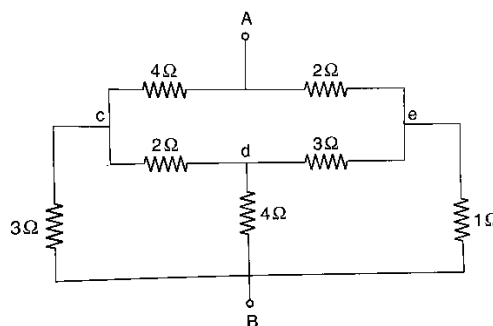


Figure -2

6. Determine current in  $XX\Omega$  resistor shown in network (figure-3) by using star delta transformation.

NOT:  $XX\Omega$  resistor would be unique/specific for each student,

example: for roll no **20TDCS024** then value of  $XX\Omega = 24\Omega$

example: for roll no **20TDCE126** then value of  $XX\Omega = 126\Omega$

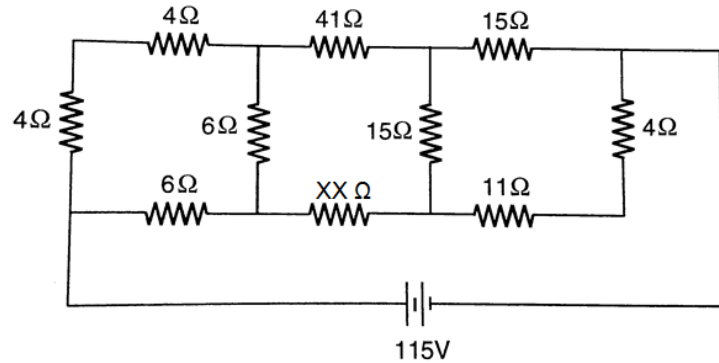


Figure-3

7. For the Circuit in Figure-4 determine the voltage across the  $20\Omega$  resistor using mesh analysis.

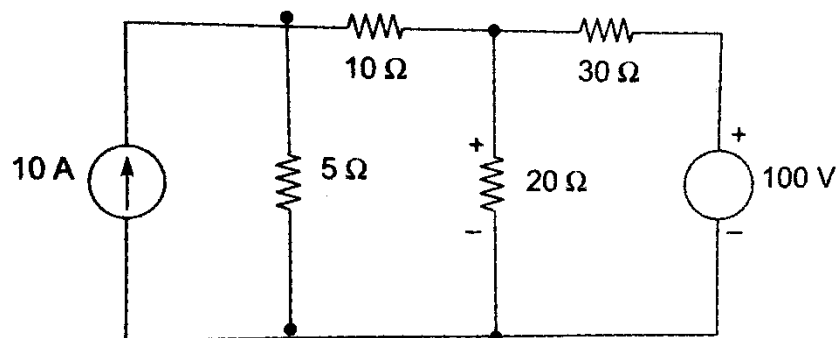


Figure-4

8. Using mesh analysis find currents  $I_1$ ,  $I_2$  and  $I_3$  for given circuit in figure-5.

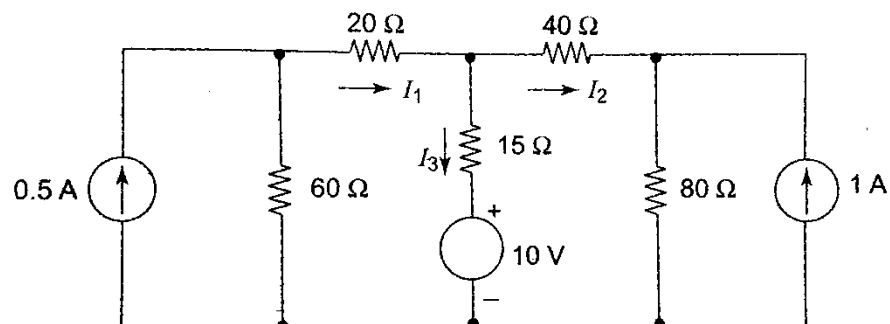


Figure-5

9. For the circuit of figure-6 determine the nodal voltages and current through  $2\Omega$  resistor.

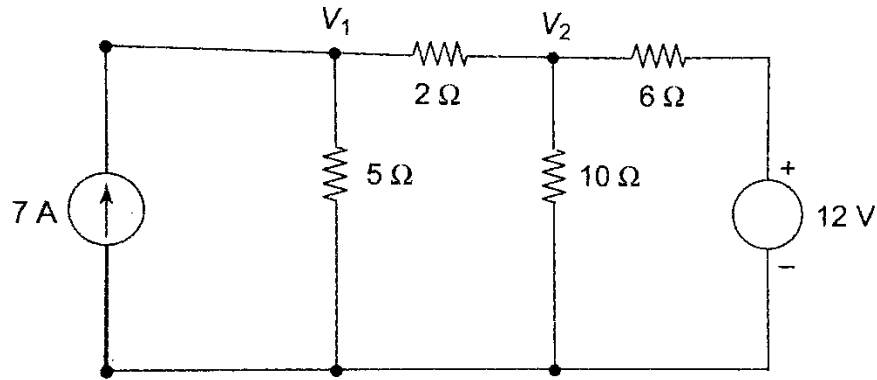


Figure-6

10. For the circuit of figure-7 determine the  $V_1$  and  $V_2$  nodal voltages.

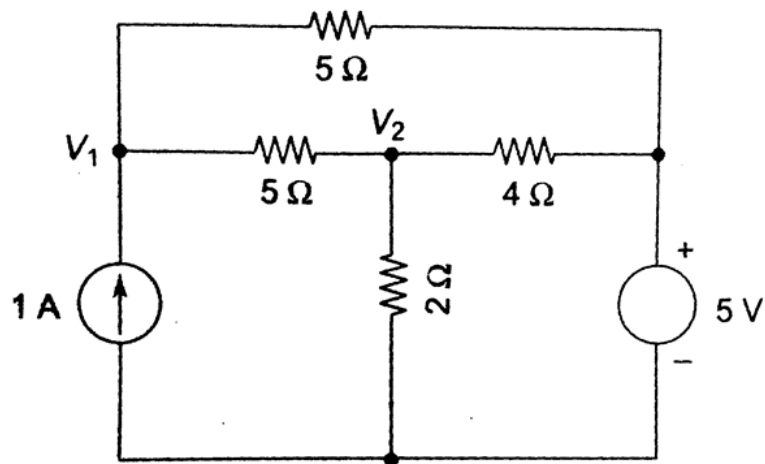


Figure-7

11. Two metal plates of area  $100\text{ cm}^2$  are separated by a dielectric of 2 mm having a relative permittivity of 5. When a dc voltage of 500V is applied across the capacitor plates, find (i) capacitance (ii) charge on the capacitor (iii) electric field strength and (iv) electric flux density.
12. A capacitor is made up of two plates with an area of  $11\text{ cm}^2$  which are separated by a mica sheet 2 mm thick. If the relative permittivity of mica is 6, find its capacitance. Now, if one plate is moved further to give an air gap 0.5 mm wide between the plate and mica, find the new capacitance.
13. Two plates are kept 1.5 cm apart in air and 1 kV supply is connected across them. Calculate the electric field strength in air when a glass sheet 0.5 cm thick with relative permittivity 3 is introduced between the plates without changing the previous distance between the plates.